

MODULE - 2.

Operational Amplifiers and Oscillators.

Syllabus:


Operational amplifiers: operational amplifier parameters, operational amplifier characteristics, operational amplifier configurations, operational amplifier circuits.

Oscillators: Barkhausen criterion, sinusoidal and non-sinusoidal oscillators, Ladder network oscillator, Wien bridge oscillator, Multivibrators, single-stage astable oscillator, Crystal controlled oscillators.


Operational Amplifiers:

- An operational amplifier is a high-gain amplifier circuit with two high-impedance input terminals and one low-impedance output.
- The inputs are identified as inverting input and non-inverting input.
- The voltage gains of integrated circuit (IC) operational amplifiers are extremely high, typically 200000.

Circuit symbol and packages:

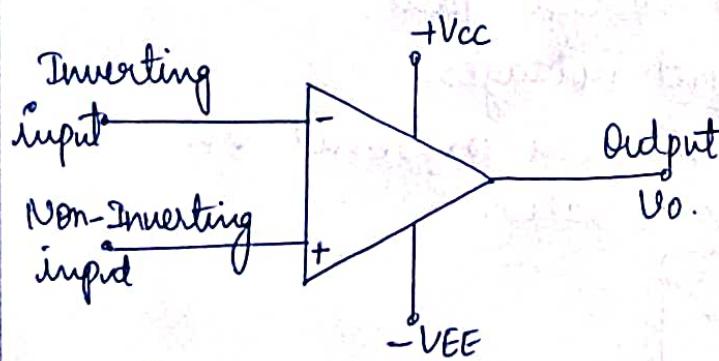

fig(a): Op-amp circuit symbol.

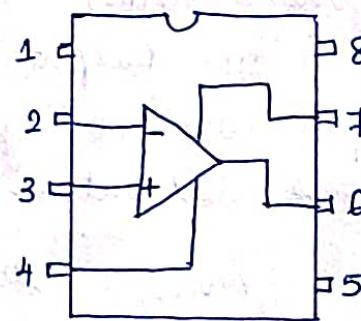

fig(b): Terminal connections for DIP Packages.

- Fig(a) shows the triangular circuit symbol for an operational amplifier. There are two input terminals, one output terminal, and two power supply terminals.
- The inputs are identified as the inverting input (-sign) and non-inverting input (+sign).
- Plus/minus supplies are normally used with Op-amps, and so the supply terminals are identified as $+V_{CC}$ and $-V_{EE}$.
- The '+' sign indicates zero phase-shift while '-' sign indicates 180° phase shift.
- Since 180° phase shift produces an inverted waveform, the '-ve' input is often referred to as the inverting input. Similarly the '+' input is known as the non-inverting input.

Operational Amplifier Parameter:

① Open-loop voltage gain:

The open-loop voltage gain of an operational amplifier is defined as the ratio of output voltage to input voltage measured with no feedback applied.

$$Av(OL) = \frac{V_{OUT}}{V_{IN}}$$

where $Av(OL)$ = open-loop voltage gain.

V_{OUT} & V_{IN} = output and input voltages.

- The open-loop voltage gain is often expressed in decibels (dB) rather than as a ratio.

$$Av(OL) = 20 \log_{10} \frac{V_{OUT}}{V_{IN}}$$

- Most operational amplifiers have open-loop voltage gain of 90 dB.

(2) Closed-loop Voltage gain:

The closed-loop voltage gain of an operational amplifier is defined as the ratio of output voltage to input voltage measured with a small proportion of the output fed back to the input.

* closed loop voltage gain is once again the ratio of output voltage to input voltage but with negative feedback applied.

Hence,

$$A_{v(CL)} = \frac{V_{out}}{V_{in}}$$

where, $A_{v(CL)}$ - open-loop voltage gain

V_{out} & V_{in} - output and input voltages.

Problem:

- * An operational amplifier operating with negative feedback produces an output voltage of $2V$ when supplied with an input of $400\mu V$. Determine the value of closed-loop voltage gain.

Soln

$$A_{v(CL)} = \frac{V_{out}}{V_{in}} = \frac{2}{400 \times 10^{-6}} = \frac{2 \times 10^6}{400}$$

$$A_{v(CL)} = 5000$$

$$A_{v(CL)} = 20 \log_{10} (5000) = 20 \times 3.7$$

$$A_{v(CL)} = 74 \text{ dB}$$

(3) Input Resistance:

The input resistance of an operational amplifier is defined as the ratio of input voltage to input current expressed in ohms.

$$R_{IN} = \frac{V_{IN}}{I_{IN}}$$

where R_{IN} - input resistance in ohms.

V_{IN} - input voltage, I_{IN} - input current.

Problem:

- An operational amplifier has an input resistance of $2M\Omega$. Determine the input current when an input voltage of 5mV is present.

Sol:

$$R_{IN} = \frac{V_{IN}}{I_{IN}}$$

Given: $R_{IN} = 2M\Omega$

$$V_{IN} = 5mV$$

$$I_{IN} = \frac{V_{IN}}{R_{IN}} = \frac{5 \times 10^{-3}}{2 \times 10^6} = 2.5 \times 10^{-9} A$$

I_{IN} = 2.5nA

Output Resistance:

The output resistance of an operational amplifier is defined as the ratio of open-circuit output voltage to short-circuit output current expressed in ohms.

- Typical values of output resistance range from less than 10Ω to around 100Ω , depending on configuration and amount of feedback employed.

$$R_{OUT} = \frac{V_{OUT}(OC)}{I_{OUT}(SC)}$$

where, R_{OUT} - output resistance in ohms

$V_{OUT}(OC)$ - open circuit output voltage.

$I_{OUT}(SC)$ - short circuit output current.

Input-offset voltage:

The voltage that must be applied differentially to the operational amplifier input in order to make the output voltage exactly zero is known as input-offset voltage.

- * Input offset voltage may be minimized by applying relatively large amounts of negative feedback.

(6) Full-power Bandwidth:

The full-power bandwidth for an operational amplifier is equivalent to the frequency at which the maximum undistorted peak output voltage swing falls to 0.707 of its low-frequency value.

- * Typical full-power bandwidths range from 10kHz - 1MHz for some high-speed devices.

(7) Slew Rate:

Slew rate is the rate of change of output voltage with time, when a rectangular step input voltage is applied.

$$\text{Slew rate} = \frac{\Delta V_{\text{out}}}{\Delta t}$$

where ΔV_{out} - change in output voltage

Δt - corresponding interval of time.

- * Slew rate is measured in V/s and typical values range from 0.2V/ μ s to over 20V/ μ s.

OPERATIONAL AMPLIFIER CHARACTERISTICS:

The characteristics for an Ideal-operational Amplifiers are

1. The open-loop voltage gain should be very high (ideally infinite)
2. The input resistance should be very high (ideally infinite)
3. The output resistance should be very low (ideally $Z_{\text{out}} = 0$)
4. Full-power Bandwidth should be as wide as possible.
5. Slew-rate should be as large as possible.
6. Input offset should be as small as possible.

Problem (Slew-rate)

1. A perfect rectangular pulse is applied to the input of an operational amplifier. If it takes $4\mu s$ for the output voltage to change from $-5V$ to $+5V$. determine the slew rate of the device.

$$\text{Slew rate} = \frac{\Delta V_{\text{out}}}{\Delta t} = \frac{10V}{4\mu s}$$

$$\text{Slew rate} = 2.5V/\mu s$$

2. A wideband operational amplifier has a slew-rate of $15V/\mu s$. If the amplifier is used in a circuit with a voltage gain of 20 and a perfect step input of $100mV$ is applied to its input, determine the time taken for the output to change level.

Soh The output voltage change will be $20 \times 100 = 2000mV$


Re-arranging formula for slew-rate,

$$\Delta t = \frac{\Delta V_{\text{out}}}{\text{slew rate}} = \frac{2V}{15V/\mu s}$$


$$\Delta t = 0.133\mu s$$

OPERATIONAL AMPLIFIER CONFIGURATION:

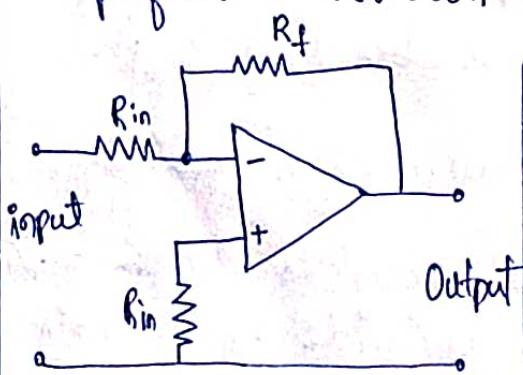
The three basic configurations for operational voltage amplifiers is shown in figure below.



a) Inverting Amplifier

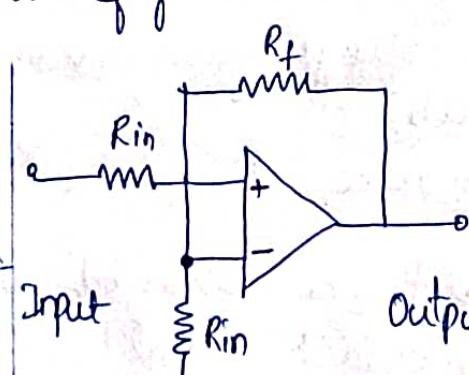

b) Non-Inverting Amplifier

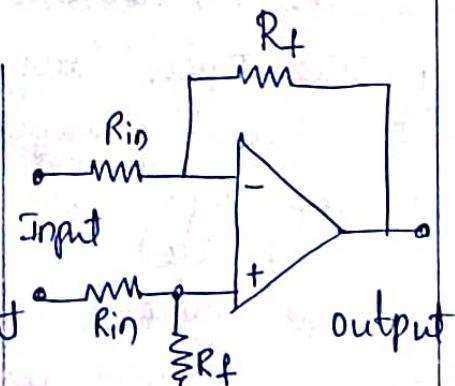

c) Differential Amplifier

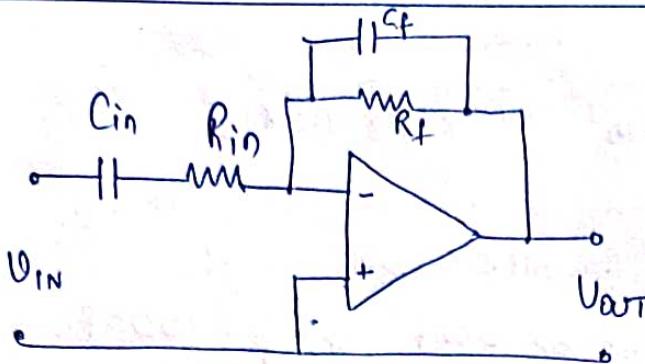


Fig: Adding Capacitors to modify the frequency response of an inverting operational amplifier.

$$R_2 = A_v \times R_1$$

$$f_1 = \frac{1}{2\pi C_{in} R_{in}} = \frac{0.159}{C_{in} R_{in}}$$

$$f_2 = \frac{1}{2\pi C_f R_f} = \frac{0.159}{C_f R_f}$$

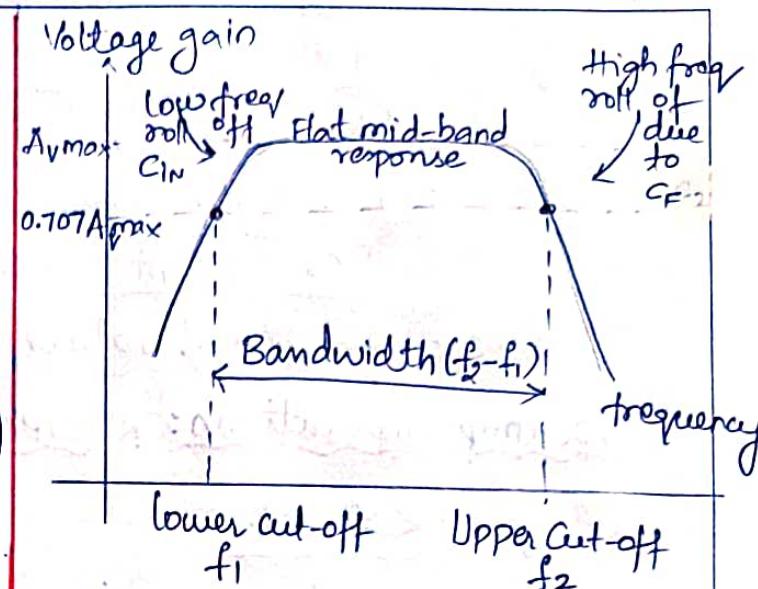


Fig: Effect of adding capacitors C_{in} and C_f to modify the frequency response of an operational amplifier.

Problem:

(1) An inverting opamp is to operate according to the following specification.

Voltage gain - 100

Input resistance (at mid-band - 10 kHz)

lower-cut-off frequency = 250 Hz

Upper-cut-off frequency = 15 kHz

Devise a circuit to satisfy the above specification using an operational amplifier.

soln

$$R_{in} = 10 \text{ k}\Omega$$

The nominal input resistance is the same as the value of R_{in}

$$A_v = \frac{R_2}{R_1}$$

$$R_2 = 100 \times 10 \text{ k}\Omega$$

$$\underline{R_2 = 1000 \text{ k}\Omega}$$

$$f_1 = \frac{0.159}{C_{in} R_{in}}$$

$$C_{in} = \frac{0.159}{f_1 R_{in}} = \frac{0.159}{250 \times 10 \times 10^3}$$

$$C_{in} = 63 \times 10^{-9} \Rightarrow C_{in} = 63 \text{ nF}$$

$$f_2 = \frac{0.159}{C_f R_f} \Rightarrow C_f = \frac{0.159}{f_2 R_{in}} = \frac{0.159}{15 \times 10^3 \times 100 \times 10^{-3}}$$



$$C_f = 0.106 \times 10^{-9}$$

$$\boxed{C_f = 106 \text{ pF}}$$

choose preferred values C_{in} as 68nF & $C_f = 100 \text{ pF}$.

OPERATIONAL AMPLIFIER CIRCUITS:

① Voltage Follower:

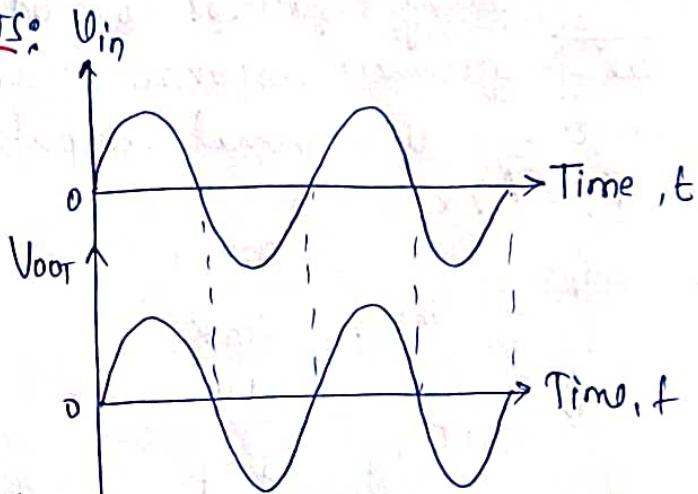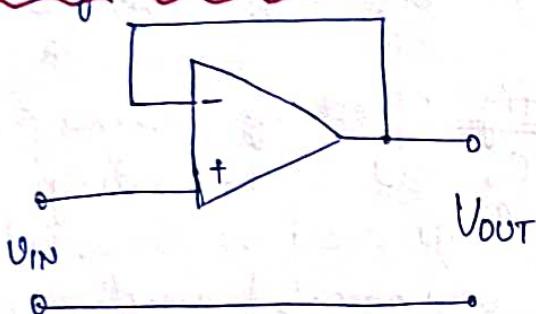

- * This circuit is essentially an inverting amplifier in which 100% of the output is fed back to the input.
- * The amplifier has an unity voltage gain, a very high input and output resistance. $\boxed{V_o = V_{in}}$ $\boxed{A_v = 1}$.

② Differentiators:


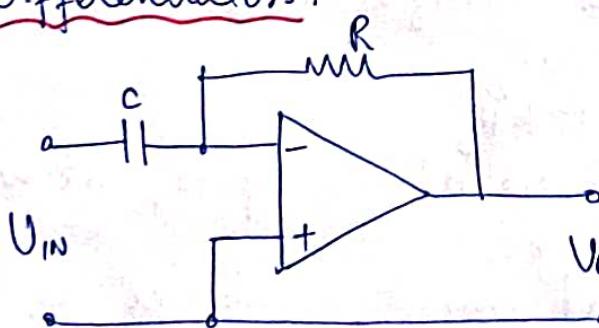


fig: Differentiator

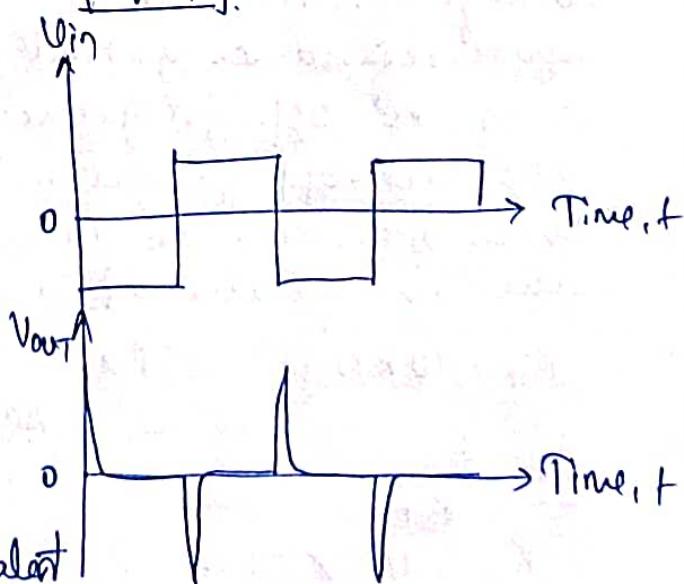

- * A differentiator produces an output voltage that is equivalent to the rate of change of its input.
- * The square wave input is converted to a train of short duration pulses at the output.

(3)

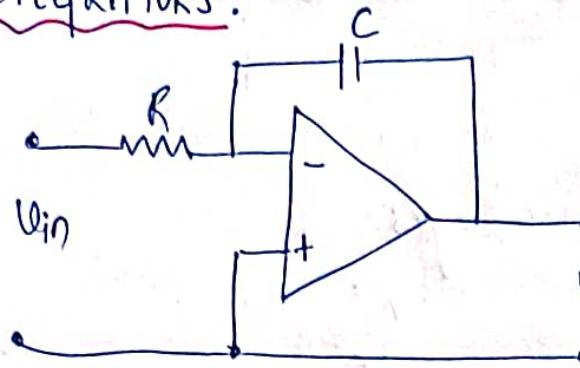
INTEGRATORS:

fig: An Integrator

- * This circuit provides the opposite function to that of a differentiator. The output voltage ramp up or down according to the polarity of the input.

 V_{in} V_{out} V_{out}

is connected in inverting mode, the output voltage is given by,

$$V_{\text{OUT}} = -(V_1 + V_2)$$

where V_1 and V_2 are input voltages.


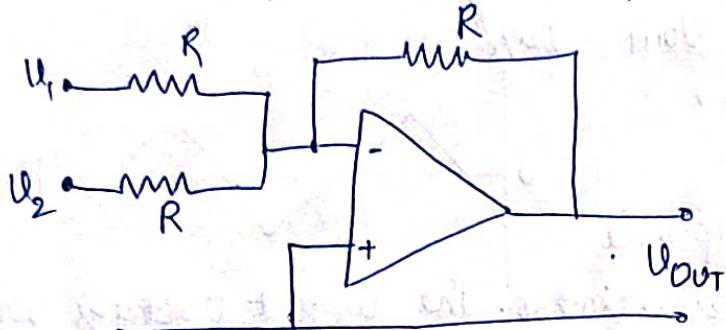


fig: A Summing Amplifier

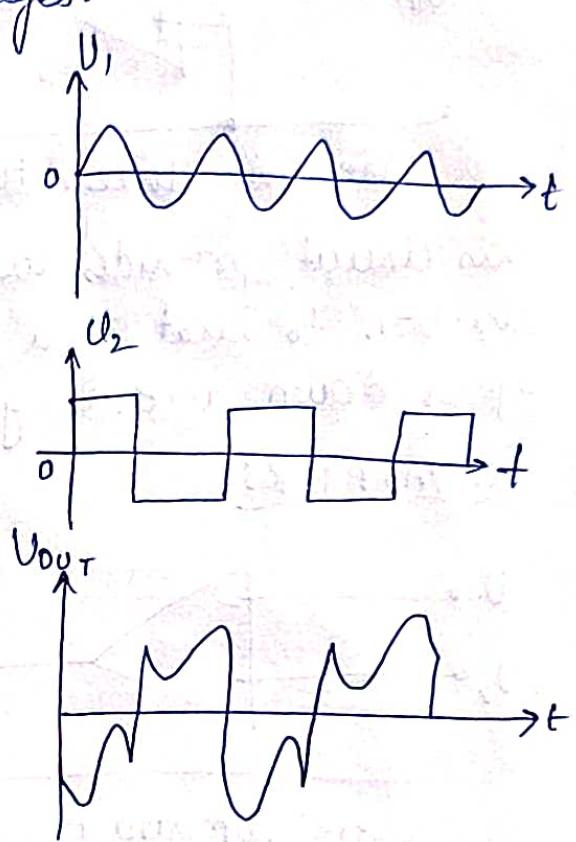

Sinusoidal and Non-Sinusoidal Oscillators:

Sinusoidal oscillator:

- A sinusoidal oscillator is an oscillator that generates a periodic signal in the shape of a sinusoidal wave.
- Types:
 - * Tuned circuit oscillators - Hartley, Colpits Oscillators.
 - * RC Oscillators - Wien bridge oscillators.
 - * Crystal oscillators - Crystal Oscillator made up of Quartz crystal.

Non-Sinusoidal oscillator:

- The oscillators that produce an output having a square, rectangular or saw-tooth waveform are called non-sinusoidal oscillators.

Multivibrators:

- Single-stage Astable oscillator
- Crystal controlled oscillator.

OSCILLATORS: It is an electronic source of alternating current or voltage having sine, square or triangular shapes.

POSITIVE FEEDBACK: Sawtooth or Pulse shapes.

An alternative form of feedback, where the output is fed back in such a way as to reinforce the input is known as positive feedback.

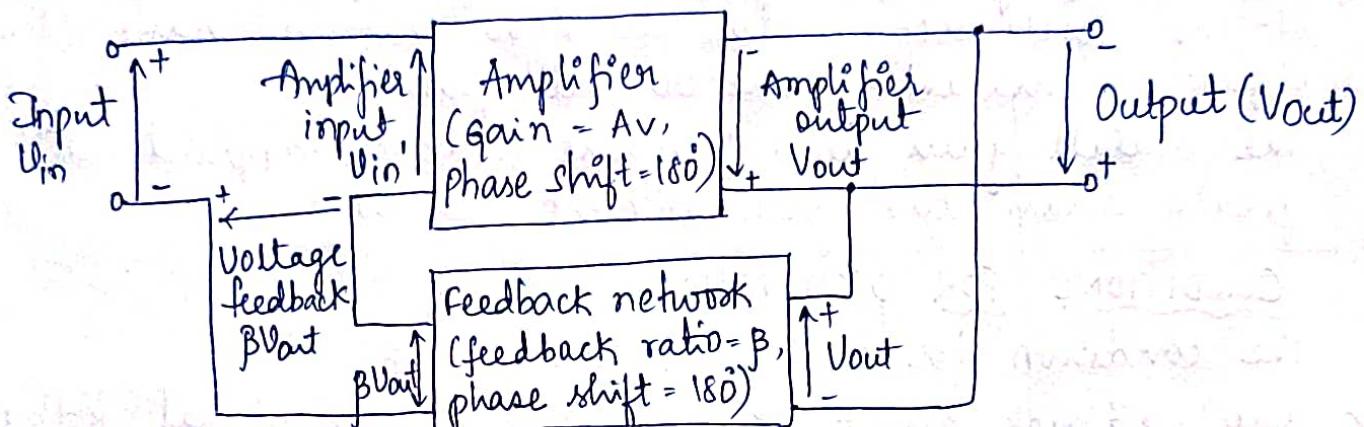


fig: Amplifier with positive feedback applied.

- * The figure above shows the block diagram of an amplifier stage with positive feedback applied.
- * Note that the amplifier provides a phase shift of 180° and the feedback network provides a further 180° . Thus the overall phase shift is 0° . The overall voltage gain G is given by,

$$\text{Overall gain, } G = \frac{V_{out}}{V_{in}}$$

By applying Kirchoff's voltage law

$$V_{in}' = V_{in} + \beta V_{out}$$

Thus, $V_{in} = V_{in}' - \beta V_{out}$

and $V_{out} = A_v, V_{in}$

where A_v - internal gain of the amplifier.

$$\text{Overall gain, } G = \frac{A_v \cdot V_{in}'}{V_{in}' - \beta V_{out}} = \frac{A_v \cdot V_{in}'}{V_{in}' - \beta (A_v \times V_{in}')}$$

Thus,
$$G = \frac{A_v}{(1 - \beta A_v)}$$

- * when loop gain βA_v approaches Unity, the denominator $(1 - \beta A_v)$ will become close to zero. This will have the effect of increasing the overall gain.
- * The overall gain with positive feedback applied will be greater than the gain without feedback.

CONDITIONS FOR OSCILLATION:

The condition for oscillation are:

- 1) the feedback must be positive (i.e., the signal feedback must arrive back in-phase with the signal at the input).
- 2) the overall loop voltage gain must be greater than 1. (i.e., the amplifier's gain must be sufficient to overcome the losses associated with any frequency selective feedback network).
- * A number of circuits can be used to provide 180° phase shift, one of the simplest being a three stage C-R ladder network that we shall meet next.

LADDER NETWORK OSCILLATOR:

- * A simple phase-shift oscillator based on a three stage C-R ladder network is shown below,
- * TR_1 operates as a conventional common-emitter amplifier stage with R_1 and R_2 providing base bias potential and R_3 and C_1 providing emitter stabilization.

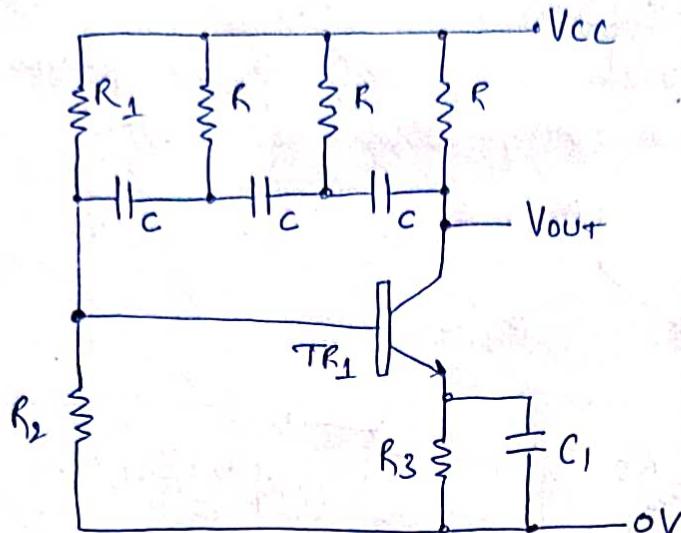


fig: Sine wave oscillator based on three stage C-R ladder network.

- * The total phase shift provided by the C-R ladder network (connected between collector and base) is 180° at the frequency of oscillation.
 - * The transistor provides the other 180° phase shift in order to realize an overall phase shift of 360° or 0° .
 - * The frequency of oscillation of the circuit is
- $$f = \frac{1}{2\pi\sqrt{6}CR}$$
- * The loss associated with the ladder network is 29, thus the amplifier must provide a gain of at least 29 in order for the circuit to oscillate.

Problem

- * Determine the frequency of oscillation of a three-stage ladder network oscillator in which $C=10\text{nF}$ and $R=10\text{k}\Omega$

Soln: Given $C=10\text{nF}$, $R=10\text{k}\Omega$

$$f = \frac{1}{2\pi\sqrt{6}CR} = \frac{1}{2\pi\sqrt{6} \times 10 \times 10^{-9} \times 10 \times 10^3} = \frac{10^4}{15.386}$$

$$f = 64\text{Hz}$$

WEIN BRIDGE OSCILLATOR:

- An alternative approach to providing the phase shift required is the use of a wein bridge oscillator network.

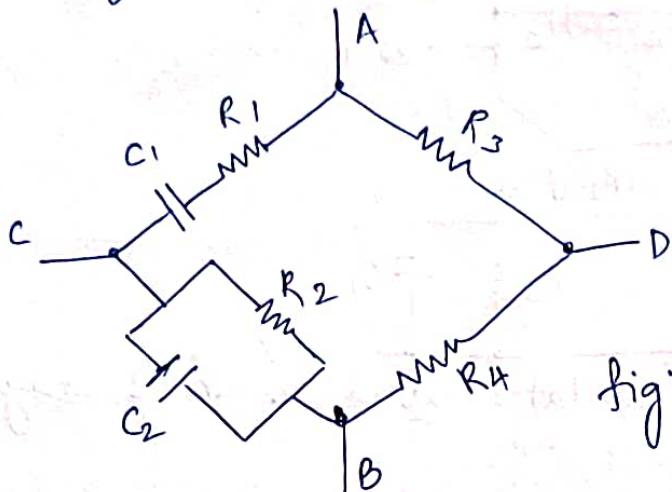


fig: A Wein Bridge networks.

- Like the C-R ladder, this network provides a phase-shift which varies with frequency.
- The input signal is applied to A and B while the output is taken from C and D.
- At one particular frequency, the phase shift produced by the network will be exactly zero. (input and output signals will be in-phase).
- If we connect the network to an amplifier producing 0° phase shift which has sufficient gain to overcome the losses of the wein bridge, oscillation will result.
- The minimum amplifier gain required to sustain oscillation is given by.

$$A_V = 1 + \frac{C_1}{C_2} + \frac{R_2}{R_1}$$

In most cases, $C_1 = C_2$ and $R_1 = R_2$, Hence the amplifier gain will be $A_V = 3$

- The frequency at which the phase-shift will be zero

is given by

$$f = \frac{1}{2\pi \sqrt{C_1 C_2 R_1 R_2}}$$

If $R_1 = R_2$ and $C_1 = C_2$


then, $f = \frac{1}{2\pi \sqrt{C^2 R^2}}$

$$f = \frac{1}{2\pi R C}$$

where $R = R_1 = R_2$ and $C = C_1 = C_2$

Problem.

Figure below shows a Wein bridge oscillator based on an operational amplifier. If $C_1 = C_2 = 100\text{nF}$. Determine the output frequencies produced by this arrangement
(a) when $R_1 = R_2 = 1\text{k}\Omega$ and (b) when $R_1 = R_2 = 6\text{k}\Omega$.

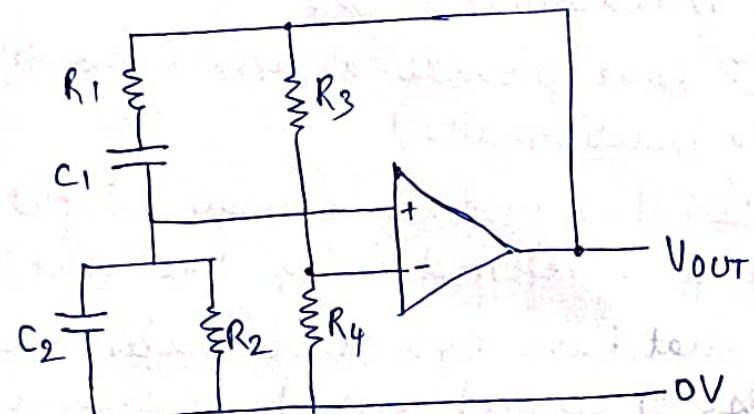

Soln: a) when $R_1 = R_2 = 1\text{k}\Omega$

where $R = R_1 = R_2$ and

$$C = C_1 = C_2$$

$$f = \frac{1}{2\pi R C} = \frac{1}{6.28 \times 100 \times 10^{-9} \times 1 \times 10^3}$$

$$f = 1.59 \text{ KHz}$$

b) When $R_1 = R_2 = 6\text{k}\Omega$

where $R = R_1 = R_2$ and

$$C = C_1 = C_2$$

$$f = \frac{1}{2\pi R C} = \frac{1}{6.28 \times 100 \times 10^{-9} \times 6 \times 10^3}$$

$$f = 265 \text{ Hz}$$

MULTIVIBRATORS:

- * There are many occasions when we require a square wave output from an oscillator rather than a sine wave output.
- * Multivibrators are a family of oscillator circuits that produce output waveforms consisting of one or more rectangular pulses.
- * The term 'Multivibrator' simply originates from the fact that this type of waveform is rich in harmonics (i.e 'multiple vibrations').
- * Multivibrators use regenerative (i.e, positive) feedback.
- * The principal types of multivibrators are
 - 1) Astable multivibrators: that provide a continuous train of pulses. (free-running multivibrators)
 - 2) Monostable multivibrators: that produce a single output pulse (have one stable state and referred to as 'one-shot')
 - 3) Bistable multivibrators: that have two stable states and require a trigger pulse or control signal to change from one state to another.

SINGLE-STAGE ASTABLE OSCILLATOR:

- * A simple form of astable oscillator that produces a square wave output can be built using just one operational amplifier as shown below.

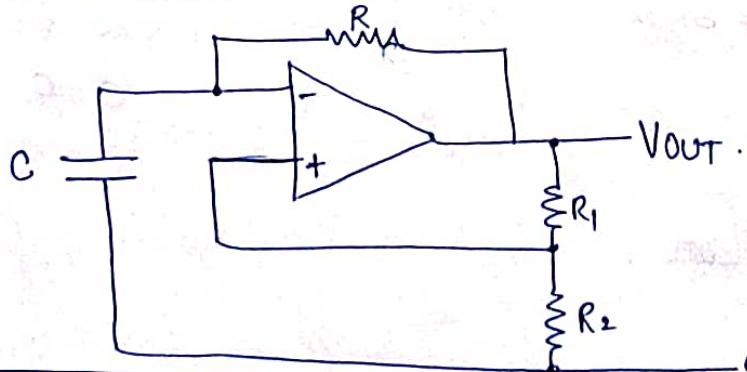


fig: Single-stage
astable Oscillator
Using op-Amps.
SVIT, Bengaluru

- * The circuit employs positive feedback with the output fed back to the non-inverting input via the potential divider formed by R_1 and R_2 .
- * This circuit can make a very simple square wave source with a frequency that can be made adjustable by replacing R with a variable or preset resistor.
- * Assume that C is initially unchanged and the voltage at the inverting input is slightly less than the voltage at the non-inverting input. The output voltage will rise rapidly to $+V_{cc}$ and voltage at the inverting input will begin to rise exponentially as capacitor C charges through R .
- * Eventually, the voltage at inverting input will have reached a value that causes the voltage at the inverting input to exceed the non-inverting input. At this point, the output voltage will rapidly fall to $-V_{cc}$. Capacitor C will then start to charge in the other direction and the voltage at the inverting input will begin to fall exponentially and process continues.
- * The Upper threshold voltage is given by

$$V_{UT} = V_{cc} \times \frac{R_2}{R_1 + R_2}$$

- * The lower threshold voltage is given by

$$V_{LT} = -V_{cc} \times \frac{R_2}{R_1 + R_2}$$

- * Finally, the time for one complete cycle of the output waveform produced by the astable oscillator is given by

$$T = 2CR \ln \left[1 + 2 \left(\frac{R_2}{R_1} \right) \right]$$

CRYSTAL CONTROLLED OSCILLATORS:

- A requirement of some oscillators is that they accurately maintain an exact frequency of oscillation.
- * In such cases, a quartz crystal can be used as the frequency determining element. The Quartz Crystal vibrates whenever a potential difference is applied across its faces. The frequency of oscillation is determined by the crystal's 'cut' and physical size.
- Most Quartz Crystals can be expected to stabilize the frequency of oscillation of a circuit to within a few parts in a million.
- * Crystals can be manufactured for operation in fundamental mode over a frequency range extending from 100kHz to around 20MHz and for overtone operation from 20MHz to well over 100MHz.
- Figure below shows a simple crystal oscillator circuit in which the crystal provides feedback from the drain to the source of a junction gate FET

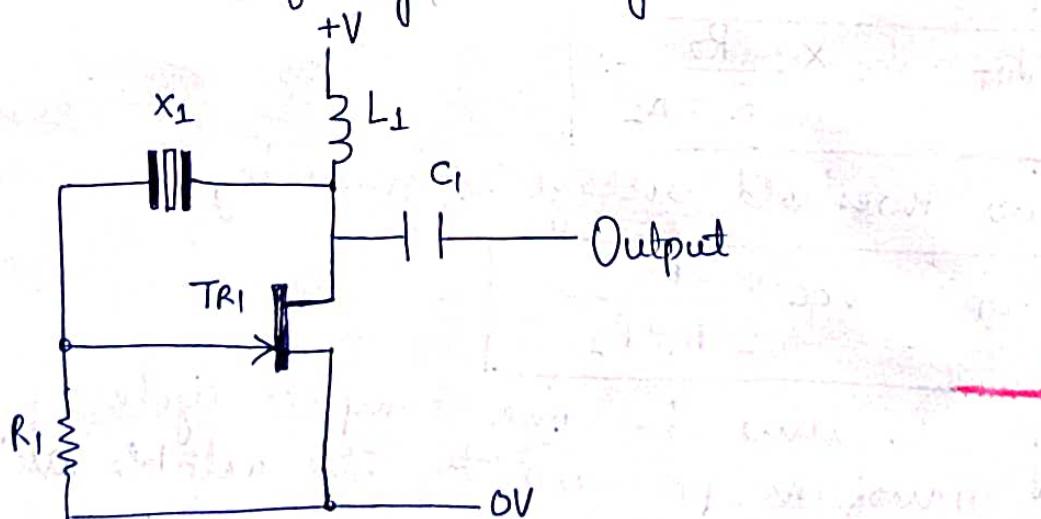


fig: A Simple JFET Oscillator.